

High DR ADC for LHC

Sarthak Kalani

Last updated: 03/31/17




COLUMBIA UNIVERSITY
IN THE CITY OF NEW YORK

Columbia Integrated Systems Laboratory




Previously, with autoselect:

 

- Auto select means verilogA logic block determines whether to choose 1x gain or 4x gain, based on input.


Current status, with autoselect:

 

- Auto select means veriloga logic block determines whether to choose 1x gain or 4x gain, based on input.

Why autoselect was not working?

 - Parasitic Cap at virtual ground node gets charged and affects output by the same amount (irrespective of gain)
- When samples are combined, if 1x samples are offset by k_{1x} , then 4x samples are offset by $k_{1x}/4$
- This limits max SNDR achieved



After stage 3:

$$V_{OUT} = A \sin(\omega t) + k \cdot C_X \cdot A \cdot \omega \cdot \cos(\omega t) \cdot \Delta t$$


for gain of 1x &

$$V_{OUT} = 4A \sin(\omega t) + k \cdot C_X \cdot A \cdot \omega \cdot \cos(\omega t) \cdot \Delta t$$

for gain of 4x


Proposed solution: Introduce ASD clock

 - Autozero slope distortion (ASD) clock discharges C_x before hold clock starts.




Result: Good SNDR for autoselect!

Clock waveforms

 

Clock waveforms

 


Enough non overlap margins available


Test Strategy

- SAR only:
 - DRE clock disabled
 - DRE bias disabled
 - SAR input from outside
 - Exact power number not needed
- DRE only:
 - ADC clock disabled
 - ADC bias disabled
 - DRE output taken out
 - SAR power, negligible if SAR clock is disabled
- Both SAR and DRE:
 - The clocks to both the blocks enabled
 - Middle pins disabled
 - DRE output -> SAR -> Serializer


SAR
Test

 

DRE
Test

 

DRE
and
SAR
Test

 


Next steps and Timeline

- Start layout
- Integrate scan chain
- Connect with 12-bit ADC.
- If time permits:
 - Low frequency T&H
 - Implement calibration scheme in Matlab

S.No.	Item	Complete by
1	Layout of individual blocks	Apr 5 th , 2017
2	Top level routing, pad connections	Apr 13 th , 2017
3	Integration with SAR-ADC	Apr 20 th , 2017
4	PEX, functionality test	Apr 23 rd , 2017

Backup Slides

PCB level schematic

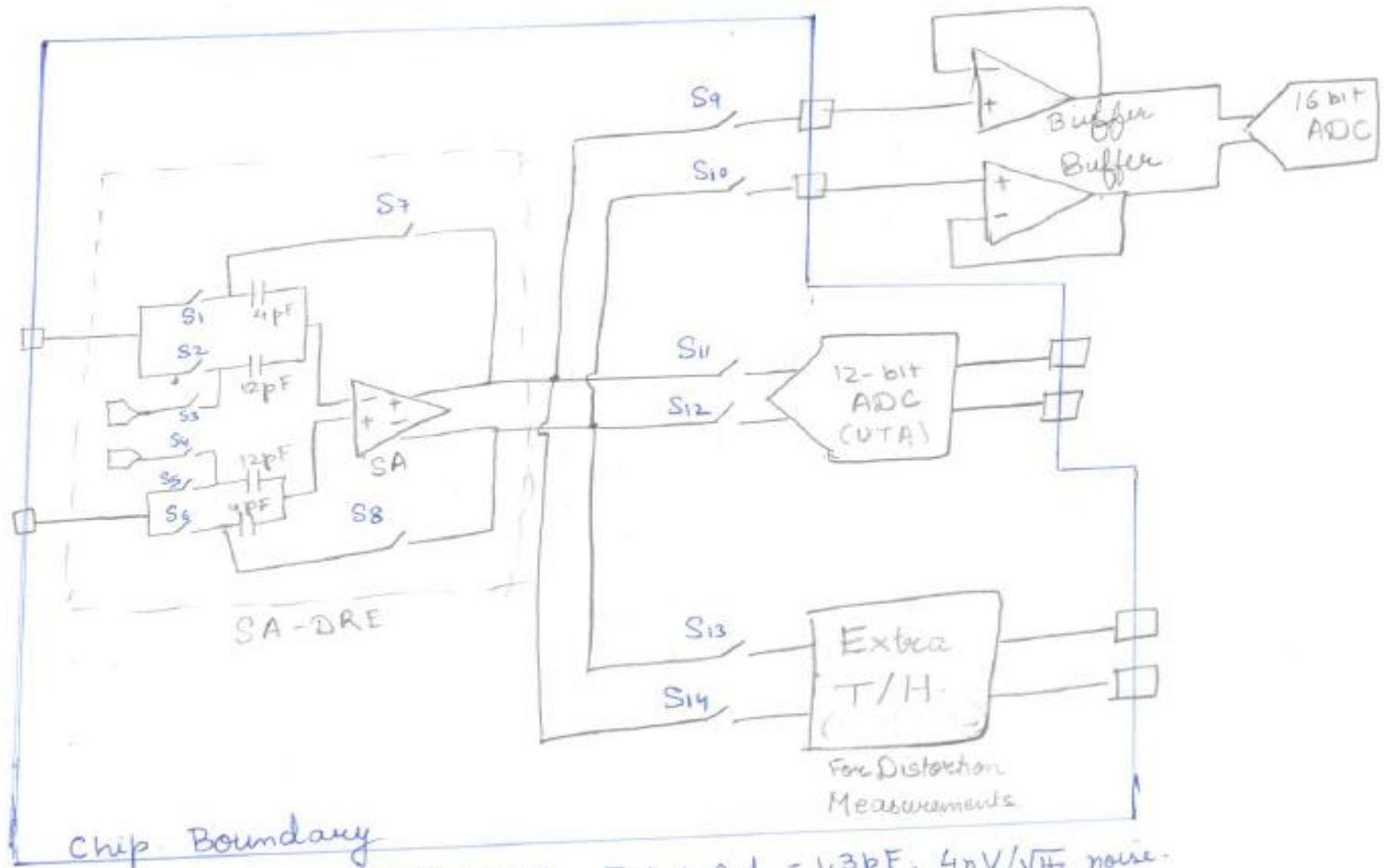

Chip Boundary


External Buffer = ADA 4817, Input cap = 1.3pF, 4nV/√Hz noise.

External ADC = AD 9650, 1.8V supply, 2.7V_{pp} output, 83dB SNDR, 25MSPS to 105MSPS




Sampling Amplifier (SA) based DRE

Small input: 4x gain


Large input: 1x gain

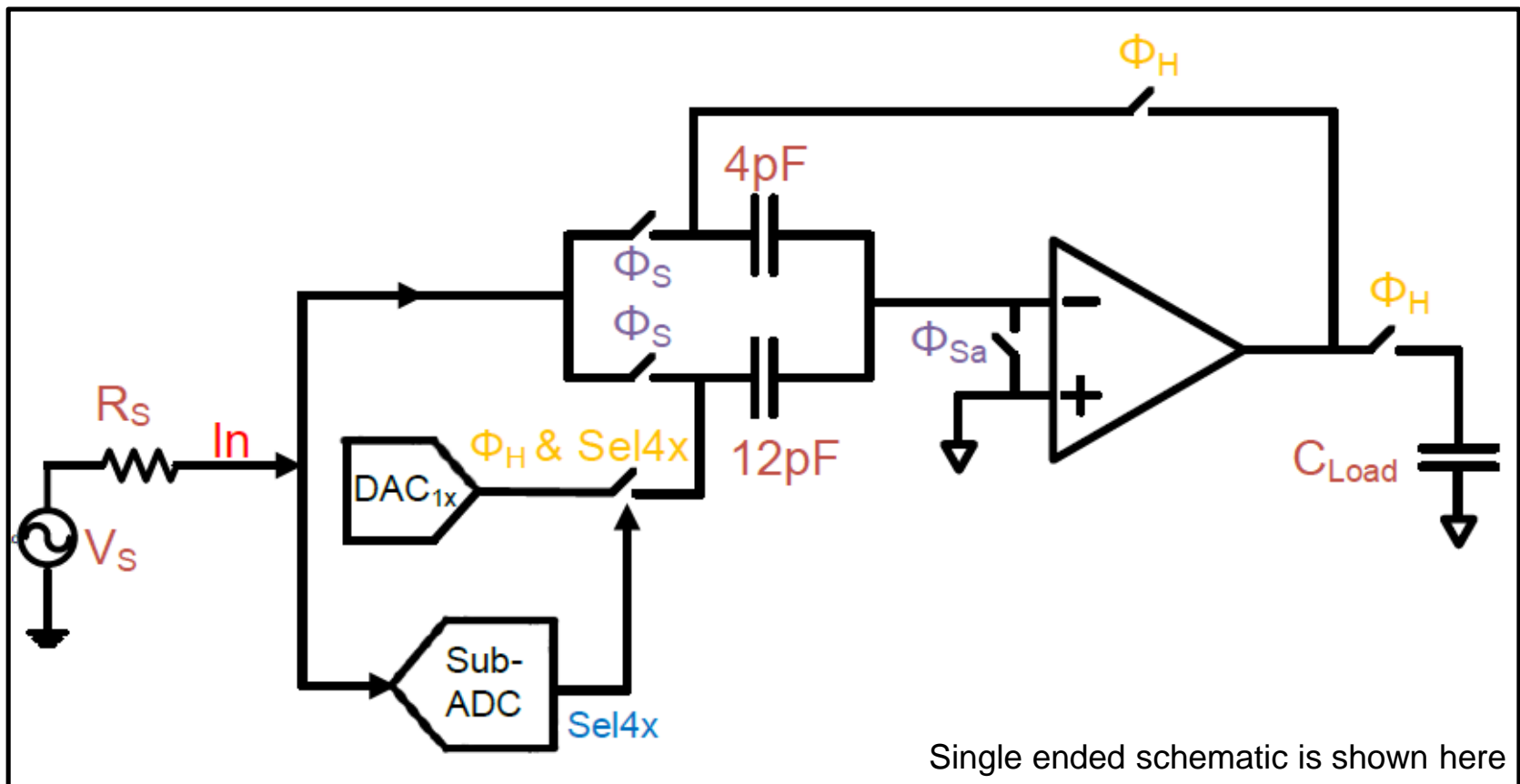


SA-DRE timing diagram

   

Sample
Phase

 


Hold Phase
&
1x Selected

 


Hold Phase
&
4x Selected

Auto select timing diagram

 

- $V_{in} = 400\text{mV}$,
- Autoselect enabled

Auto select timing diagram

 

- $V_{in} = 400\text{mV}$,
- Autoselect enabled


Manual select timing diagram

Differential
Input

Differential
Output

Br1x Select
Always
enabled

PhiS clock

 


- $V_{in} = 400\text{mV}$,
- Manselect enabled
- Branch 1x selected

Sim Results@ 5MHz Input, 40MSPS

- $1.6V_{PP}$ differential input provided, 1x gain selected manually.
 - Similar results obtained for using 4x gain at maximum value.
- Simulations contain:
 - Transistor level transient simulation
 - Transient noise enabled
 - Input resistance of 10Ω . Bond wires not added yet.
- Tt, ff, ss, sf and fs corners simulated for 0°C and 50°C
 - All results better than 68.7dB SNDR
 - **Bias currents not adjusted yet** to equalize power consumption.


Corner	SNR (dB)	SNDR (dB)	Current (mA)	Vout _{pp} (diff) (V)
tt 0	73.1	70.58	13.83	1.6
tt 50	72.38	68.7	14.6	1.6
ss0	72.33	70.7	11.96	1.6
ff 50	71.77	69.27	20.16	1.6

Current Status: With ManSel: ss0

 


- Manual select means either one of 1x gain or 4x gain is selected for the complete experiment .

Layout planning

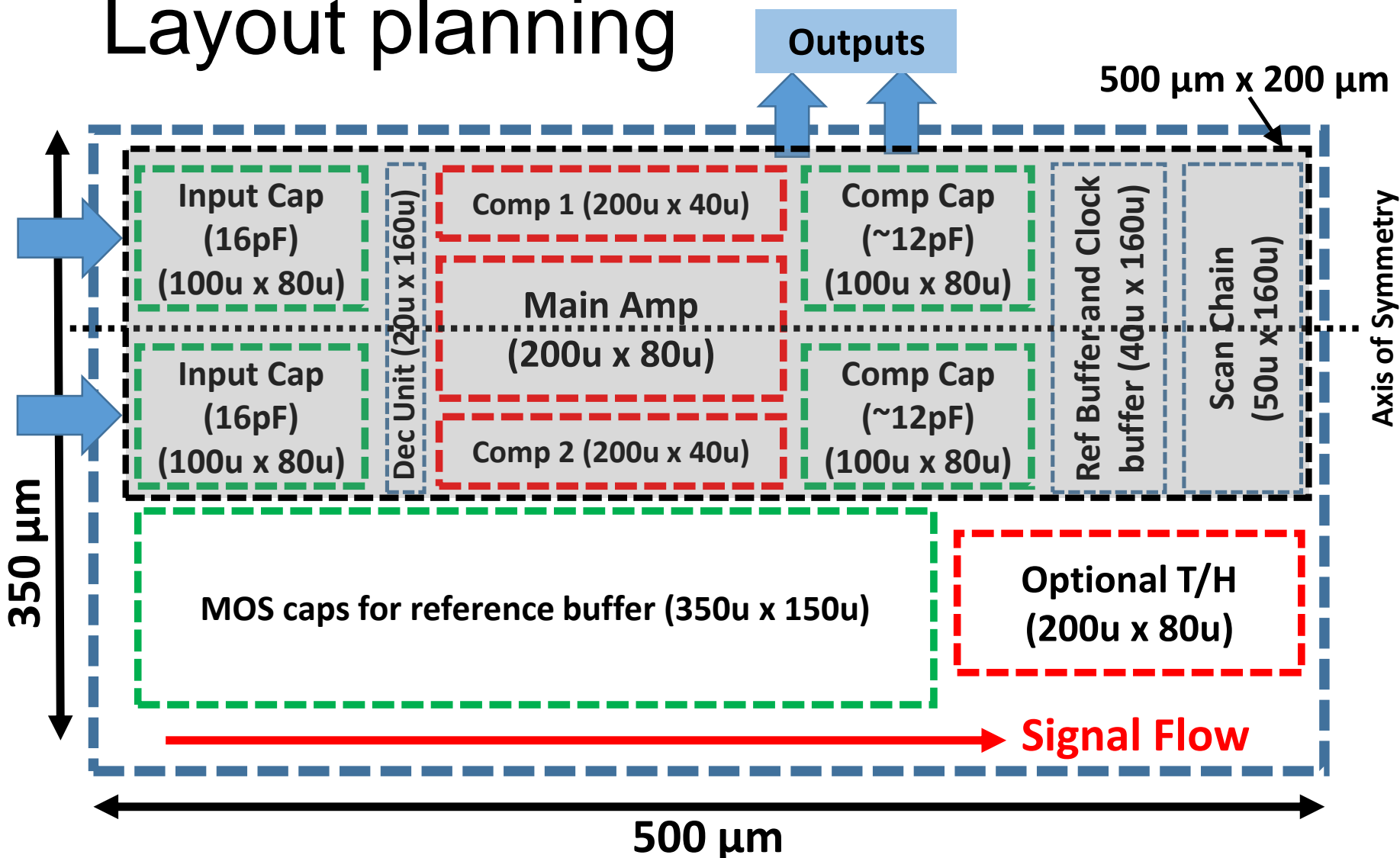


Channel area: 500 μm x 200 μm , Active area: 500 μm x 350 μm

Dual gain as DRE

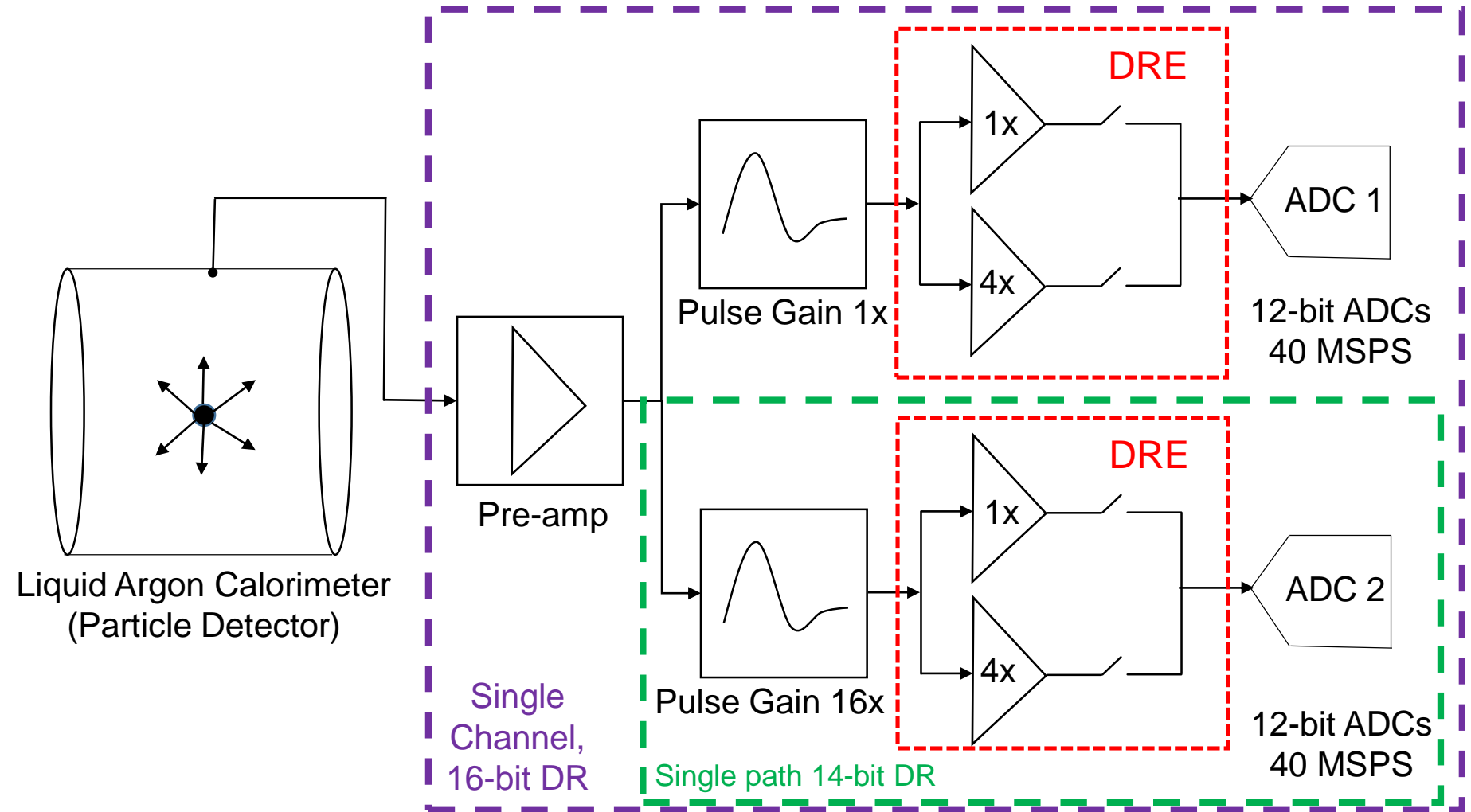

Switching selection scheme (contd.)

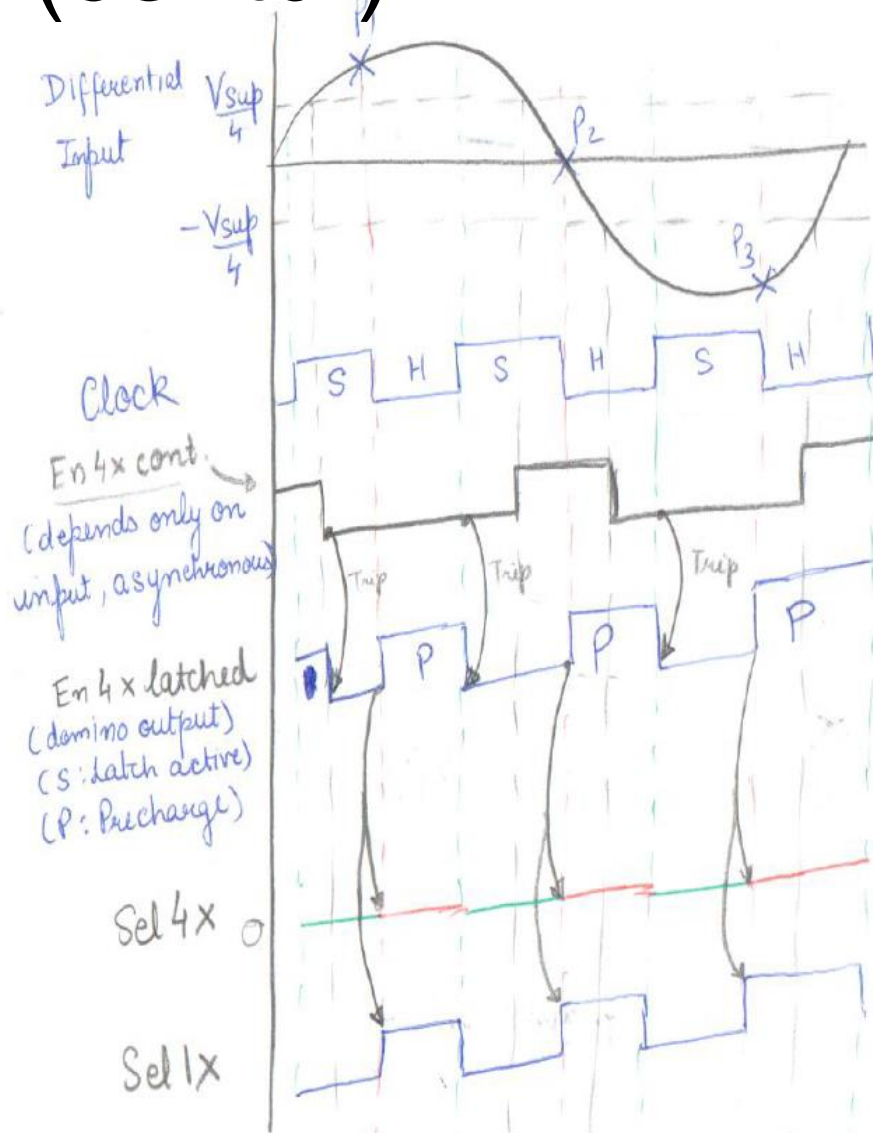

Timing


- S \Rightarrow 1x & 4x Sample
- Hadv \Rightarrow Decide 1x or 4x
- H \Rightarrow Either Sel 1x or Sel 4x becomes 1.

Selection process:


- H \Rightarrow Precharge (P) En4x latched node (output of domino latch)
- S \Rightarrow Latch active, anytime En4x cont. is 0 (zero), domino trips, output 0.
- Hadv \Rightarrow Transfer latch value to make either sel 1x active or sel 4x active
- H \Rightarrow cycle repeats
- During S, sel 1x & sel 4x are 0 (zero)

Switching selection scheme (contd.)

Case 2: Smaller input

 

Circuit Diagram:

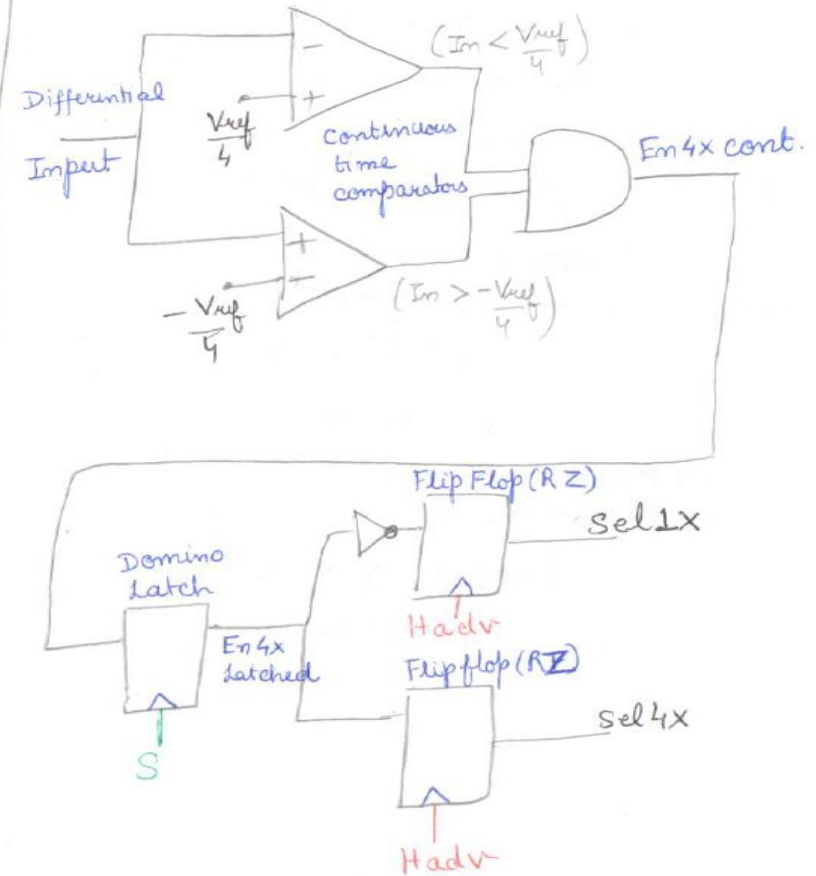

Continuous time comparators: High gain ~~low~~ amplifiers (40 dB)